

Homework 4 Solution

1. (5 points)

a. (2 points) Derive a Boolean equation for the output X

$$X = \overline{\overline{B + A} \oplus C} \overline{B(B + D)}$$

Grade guide: correct: 2; incorrect 0. It's not required to simplify this Boolean equation.

b. (3 points) Draw a truth table for the circuit

If the table is incorrect with up to 4 (or 2 for reduced table) mismatches: 2; If the table is incorrect with more than 4 mismatches: 1; no table: 0.

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

2. (3 points) Introduction to Logisim

**Grade guide: If the circuit file is submitted and correct: 3, no file: 0
Either a screenshot in file or individual submitted file is OK.**

3. (14 points) Design a combinational circuit system.

1) (3 points) x, y, and z are inputs; A, B, and C are outputs. Draw a truth table for the given function.

Grade guide: all correct 3; If the table is incorrect with up to 4 (or 2 for reduced table) mismatches: 2; If the table is incorrect with more than 4 mismatches: 1; no table: 0.

X	Y	Z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

- 2) (3 points) Based on the truth table you draw, build K-maps for the output A, B, and C.

Grade guide: each incorrect table: -1; no table at all: 0.

Table for A

	$\sim Y \sim Z$	$\sim Y Z$	$Y Z$	$Y \sim Z$
$\sim X$			1	1
X		1	1	1

Table for B

	$\sim Y \sim Z$	$\sim Y Z$	$Y Z$	$Y \sim Z$
$\sim X$	1	1		
X	1		1	

Table for C

	$\sim Y \sim Z$	$\sim Y Z$	$Y Z$	$Y \sim Z$
$\sim X$		1	1	
X	1			1

3) (3 points) Derive (as simple as possible) Boolean equations for A, B, C using the Karnaugh maps

Grade guide: each incorrect equation: -1

A = $Y + XZ$


B = $\sim X \sim Y + \sim Y \sim Z + XYZ$

C = $\sim XZ + X \sim Z$

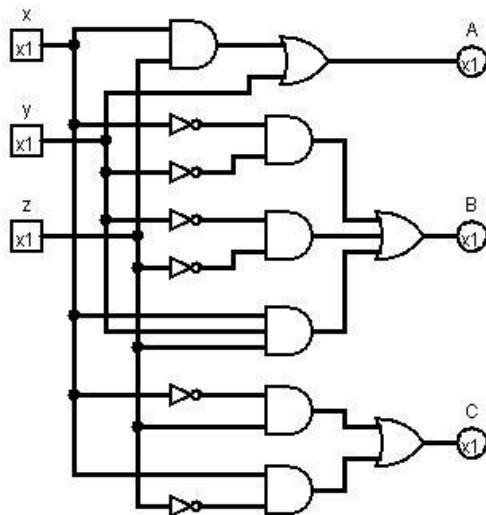4) (3 points) Based on the Boolean equations, draw the logical gate diagram (circuit) for this system in Logisim. Attach the circuit file and image.

Grade guide: If the circuit file is submitted and correct: 3, incorrect: 1, no file: 0

Either a screenshot in file or individual submitted file is OK.



5) (2 points) Test your circuit with the Logisim simulation and generate the truth table (In logisim, project-->analyze circuit-->table), and copy & past the table here.

Grade guide: no table: 0

x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0