

Homework 5 Solution

Q1. (6 points)

For each sub-question: correct: 1, incorrect: 0.5, no answer: 0.

For the K-map, there can be all different representations. So, as long as the equation is equivalent, mark it as correct.

1) A truth table for Full-Adder

x	y	z	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

2) K-map for S

	1		1
1		1	

$$S = \sim x \sim y z + \sim x y \sim z + x y z + x \sim y \sim z$$

3) K-map for C


		1	
	1	1	1

$$C = xy + yz + xz$$

$$\begin{aligned}
 4) S &= \sim x \sim y z + \sim x y \sim z + x y z + x \sim y \sim z \\
 &= \sim x (\sim y z + y \sim z) + x (y z + \sim y \sim z) \\
 &= \sim x (y \text{ XOR } z) + x \sim (y \text{ XOR } z) \\
 &= x \text{ XOR } y \text{ XOR } z
 \end{aligned}$$

5) $C = xy + yz + xz$
 $= xy + yz(x + \sim x) + xz(y + \sim y)$
 $= xy + xyz + \sim xyz + xyz + x\sim yz$
 $= xy + \sim xyz + x\sim yz$
 $= xy + (x \text{ XOR } y)z$

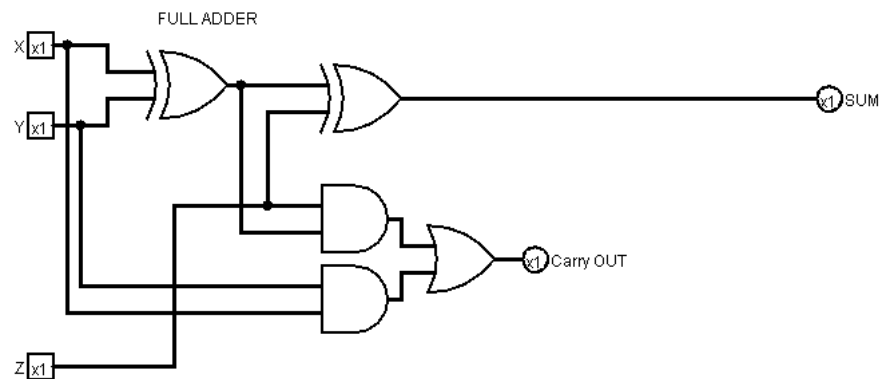6) File is not submitted: 0. Image is not attached: 0.



Q2. (6 points)

1) File is attached: 3. If there is no circuit file attached: 0

2) Complete the following truth table for the following sequential circuit:

If all correct: 3, 1~5 mistakes: 2, all other cases: 0


X	Y	Carry-in (or Q before clock)	S (before clock)	Carry-out (before clock)	S (after clock)	Carry-out (after clock)
0	0	0	0	1	1	1
0	0	1	1	1	1	1
0	1	0	1	1	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	0
1	0	1	0	0	1	1
1	1	0	0	0	0	0

1	1	1	1	0	0	0
---	---	---	---	---	---	---

Q3. (4 points)

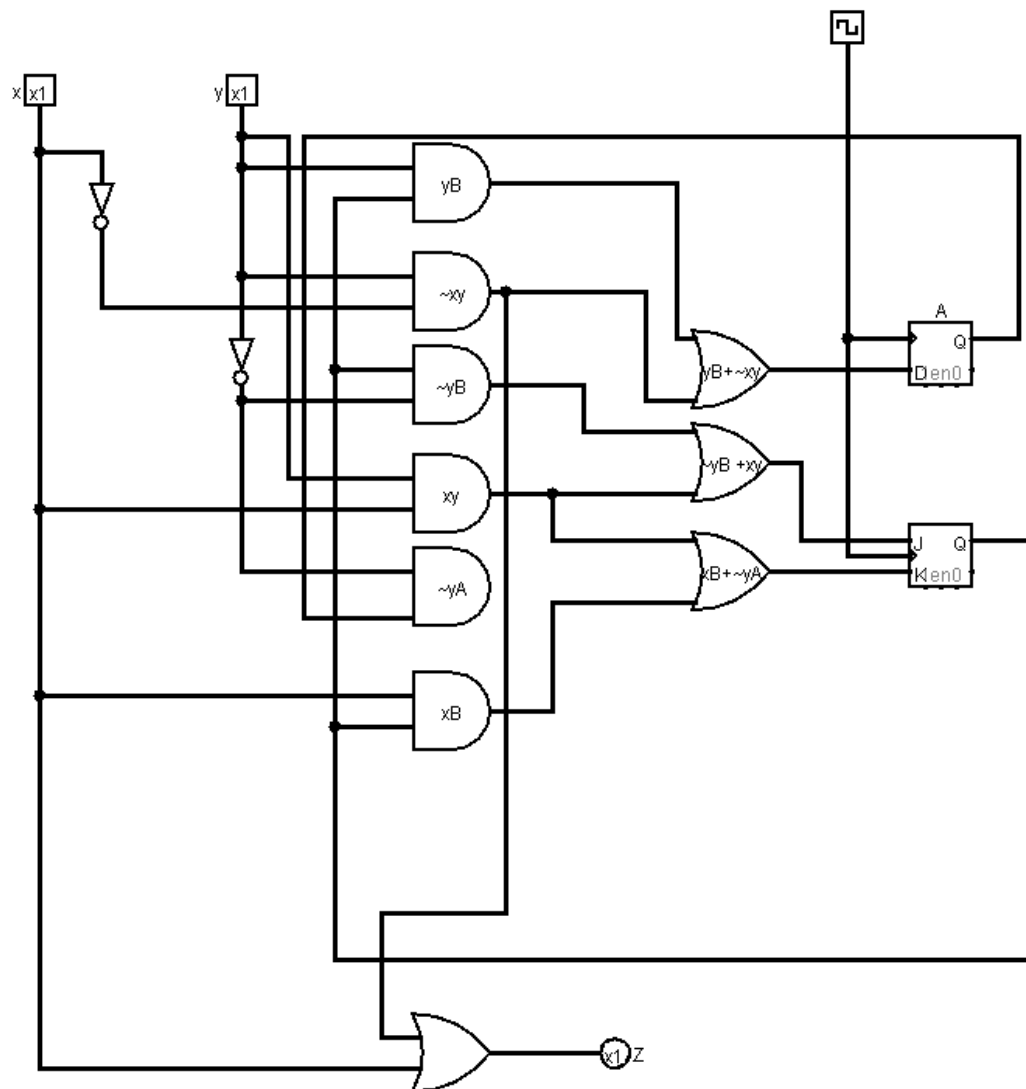
1) (2 points) Draw the logic diagram of the circuit and test it with Logisim. Copy and paste the circuit image and report the test result. (Attach the circuit file separately)

If image and circuit exist and are correct: 2, incorrect: 1, no file or image: 0



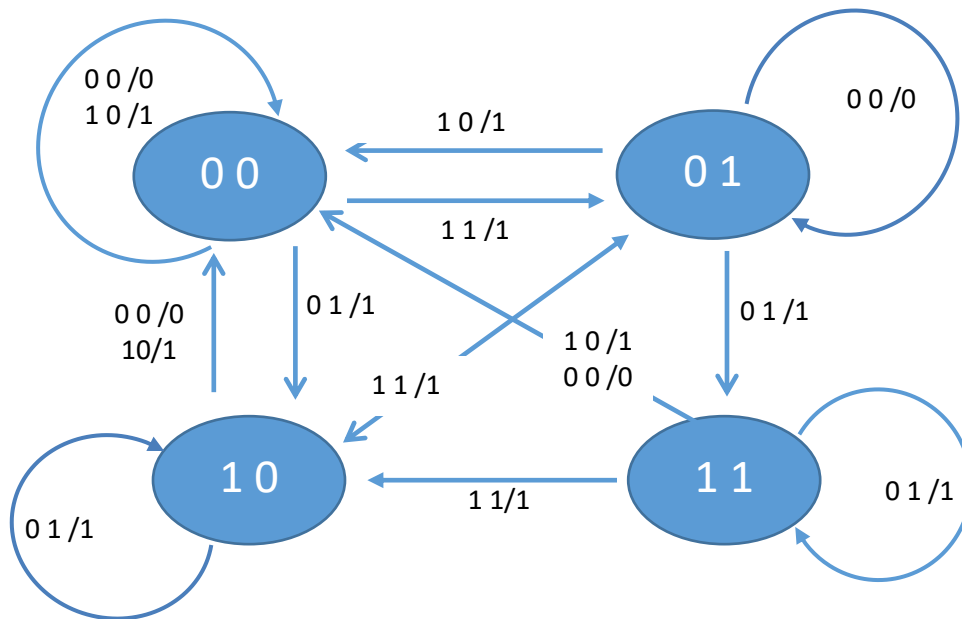
2) (2 points) If correct: 2, 1~4 mistakes: 1, more than 4 mismatches: 0.5, no diagram: 0

****took off "0.5" point each for missing input or missing output.



Q4. (10 points)

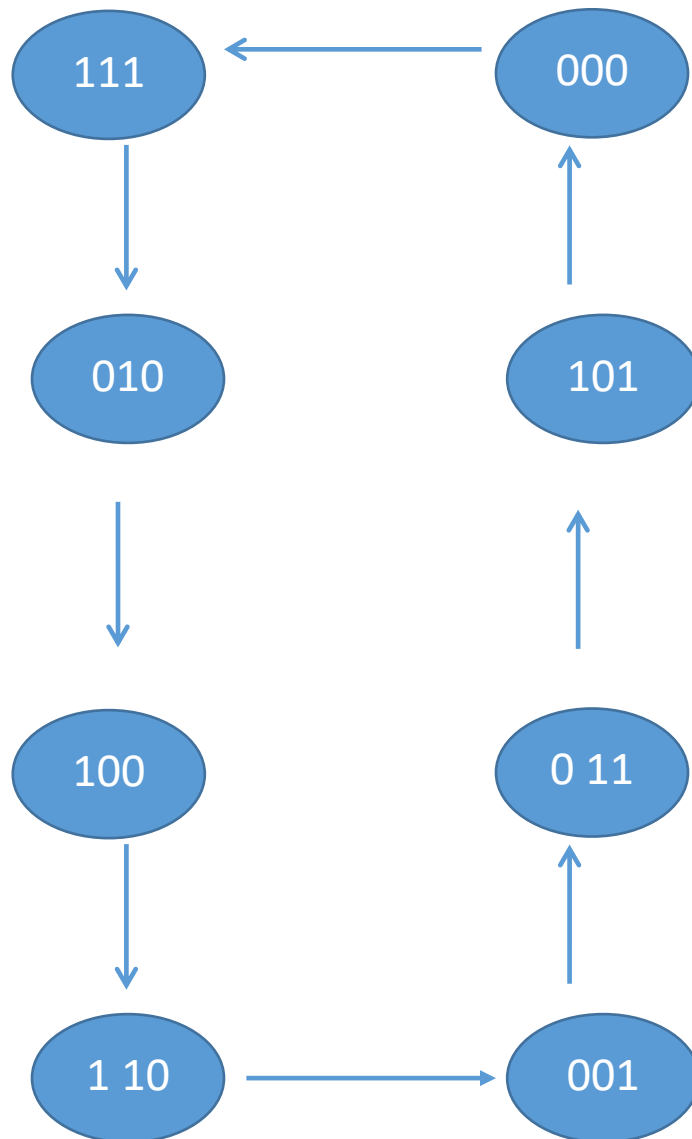1) Draw a state diagram: If correct: 2, incorrect: 1, No answer: 0



2) Construct an excitation table If correct: 2, incorrect: 1, No answer: 0

A	B	C	A_{t+1}	B_{t+1}	C_{t+1}	J_a	K_a	J_b	K_b	J_c	K_c
0	0	0	1	1	1	1	x	1	x	1	x
0	0	1	0	1	1	0	x	1	x	x	0
0	1	0	1	0	0	1	x	x	1	0	x
0	1	1	1	0	1	1	x	x	1	x	0
1	0	0	1	1	0	x	0	1	x	0	x
1	0	1	0	0	0	x	1	0	x	x	1
1	1	0	0	0	1	x	1	x	1	1	x
1	1	1	0	1	0	x	1	x	0	x	1

3) Draw K-maps and derive Boolean equations using K-maps. Make the equations as simple as possible (If correct: 2, incorrect: 1, No answer: 0)

$\sim A \sim B$

$\sim A B$

AB

$A \sim B$

$\sim C$

1	1	x	x
	1	x	x

C

$$J_a = B + \sim C$$

$\sim A \sim B$

$\sim A B$

AB

$A \sim B$

$\sim C$

x	x	1	
x	x	1	1

C

$$K_a = B + C$$

$\sim A \sim B$
 $\sim A B$
 AB
 $A \sim B$

$\sim C$	1	x	x	1
C	1	x	x	

$$J_b = \sim A + \sim C$$

$\sim A \sim B$
 $\sim A B$
 AB
 $A \sim B$

$\sim C$	x	1	1	x
C	x	1		x

$$K_b = \sim A + \sim C$$

$\sim A \sim B$
 $\sim A B$
 AB
 $A \sim B$

$\sim C$	1		1	
C	x	x	x	x


$$J_c = \sim A \sim B + AB$$

$\sim A \sim B$
 $\sim A B$
 AB
 $A \sim B$

$\sim C$	x	x	x	x
C			1	1

$$K_c = A$$

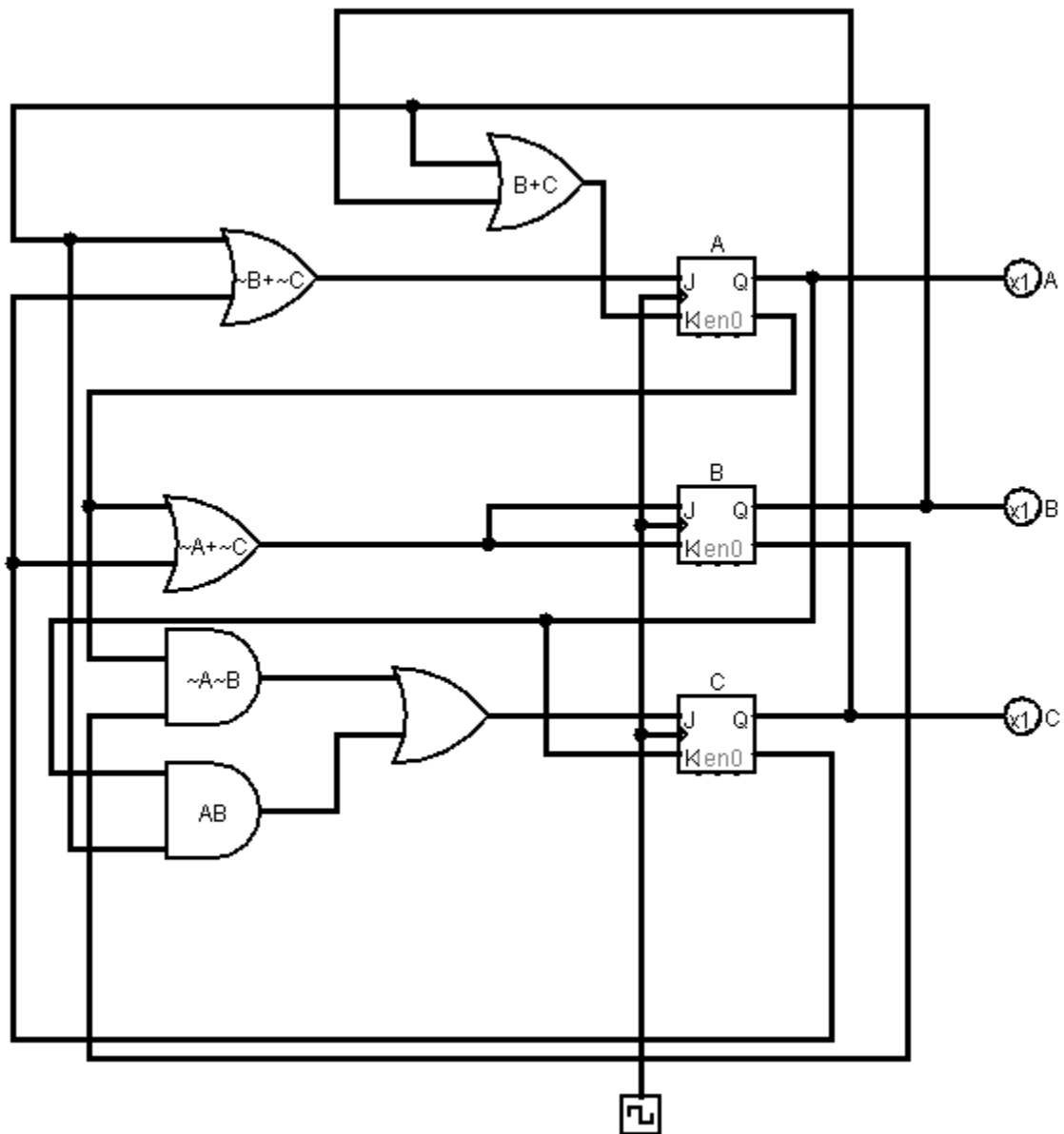- 4) If there is neither image nor circuit: 0; incorrect image or circuit 1; both correct 2.



- 5) If no table: 0

Q5. (2 points)

- 1) Suppose you want to write a data 1 0 1 to the word 3 (address 3). Give the correct values of S1, S0, Bit2, Bit1, Bit0, ~WE, reset, for this task, and test it with the circuit.

RESET	S1	S0	Bit2	Bit1	Bit0	~WE
0	1	1	1	0	1	1

Correct: 1, Incorrect: 0.5, No answer: 0.

- 2) Suppose you want to read a data from the address 1. Give the correct values of S1, S0, Bit2, Bit1, Bit0, ~WE, reset, for this task.

RESET	S1	S0	Bit2	Bit1	Bit0	~WE
0	0	1	x	x	x	0

Correct: 1, Incorrect: 0.5, No answer: 0.