

Bisrat Asefaw
 CSS 422 (Hardware)
 Prof. Yang

Homework Problem Set #5

Q1. (6 points) A full adder is a combinational circuit that forms the arithmetic sum of three input bits. It consists of three inputs, x, y, z, and two outputs, C and S. Two of the input, that is, x and y, represent the two significant bits to be added. The third input, z, represents the carry from the previous lower significant position. The output S denotes the sum of two bits and C denotes carry. Answer the following sub-questions.

1) Construct a truth table for the Full-Adder

x	y	z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

2) Based on the truth table, construct a K-map for the output S and derive a Boolean equation using K-map. Make the equation as simple as possible.

S table	xy	$\sim xy$	$\sim x \sim y$	$x \sim y$
z			1	
$\sim z$		1		1

$$S = \sim x \sim y z + \sim xy \sim z + x \sim y \sim z$$

3) Based on the truth table, construct a K-map for the output C and derive a Boolean equation using K-map. Make the equation as simple as possible.

C table	xy	$\sim xy$	$\sim x \sim y$	$x \sim y$
z	1	1		1
$\sim z$	1			

$$C = xy + yz + xz$$

4) By algebraic manipulation, show that S can be expressed as the exclusive-OR of the three input variables. That is, show that,

$$S = x \text{ XOR } y \text{ XOR } z.$$

You can prove by deriving from $S = x \text{ XOR } y \text{ XOR } z$ to the answer you got in the question 2)


$$\begin{aligned} S &= x \text{ XOR } z \text{ XOR } y \\ &= (\sim(x \text{ XOR } y)z) + (x \oplus y)\sim z \\ &= (\sim(x\sim y + \sim x y)z) + ((x\sim y + \sim x y)\sim z) \\ &= (x\sim y\sim z + \sim x y\sim z) + (\sim(x\sim y + \sim x y)z) \\ &= (\sim(x\sim y) * \sim(\sim x y))z + \sim x y\sim z + x\sim y\sim z \\ &= ((x + \sim y) * (\sim x + y))z + \sim x y\sim z + x\sim y\sim z \\ &= (x\sim x + x y + \sim x\sim y + y\sim y)z + \sim x y\sim z + x\sim y\sim z \\ &= (x y + \sim x\sim y)z + \sim x y\sim z + x\sim y\sim z \\ &= \underline{\underline{xy z + \sim x \sim y z + \sim x y \sim z + x \sim y \sim z}} \end{aligned}$$

5) By algebraic manipulation, show that C can be expressed as the following term $C = xy + (x \text{ XOR } y)z$.

$$xy + (x \text{ XOR } y)z = xy + (x\sim y + \sim x y)z$$


$$\begin{aligned} &= xy + x\sim y z + \sim x y z \text{ (Note: } xy = xyz + xy\sim z) \\ &= xyz + xy\sim z + x\sim y z + \sim x y z \\ &= x(yz + y\sim z + \sim y z) + \sim x y z \\ &= x(y + z) + \sim x y z \text{ (Note: } y = yz + y\sim z = y; z = yz + \sim y z, \text{ so } yz + y\sim z + yz + \sim y z, \text{ while } yz + yz = yz) \\ &= xy + xz + \sim x y z + xyz \text{ (Note: Since } xy + xz \text{ is here } xyz \text{ is logically inferred as here)} \\ &= xy + xz + yz(x + \sim x) \\ &= \underline{\underline{xy + xz + yz}} \end{aligned}$$

 6) Based on 4) and 5), draw a circuit for the full-adder in Logisim simulator, **attach the image file and submit the circuit file!**



Q2. (6 points) The following sequential circuit includes a full adder (described in the previous question). Inputs are X, Y and carry-in, and outputs are the next state of S and Q.

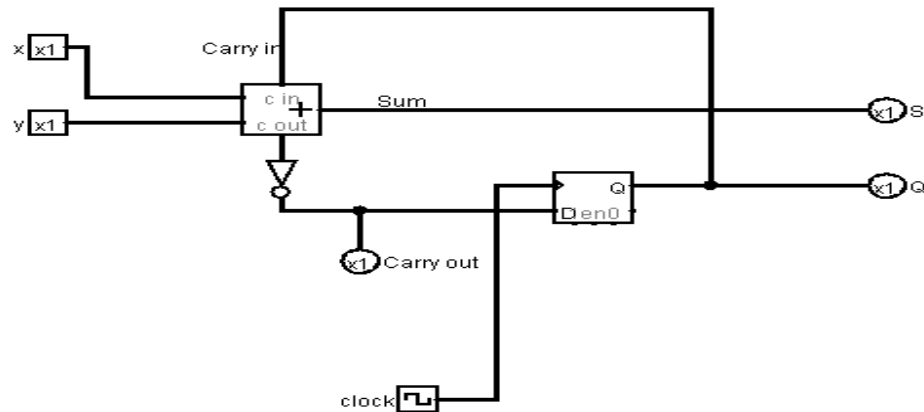1) Implement the sequential circuit in Logisim simulator and **submit the circuit file**.



2) Complete the following truth table for the following sequential circuit: Note that the Carry out signal is an output, not an input. The carry in signal is the same as the Q. You can change the Carry-in bit by clicking the D-FF.

X	Y	Carry-in (or Q before clock)	S (before clock)	Carry-out (before clock)	S (after clock)	Carry-out (after clock)
0	0	0	0	1	1	1
0	0	1	1	1	1	1
0	1	0	1	1	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	0
1	0	1	0	0	1	1
1	1	0	0	0	0	0
1	1	1	1	0	0	0

Q3. (4 points) A sequential circuit has one D flip-flop and one JK flip-flop, two inputs x and y, and one output z. A is the output of D flip-flop, and B is the output of JK-flip-flop; A and B together form the "output state" of the circuit. The flip-flop *input* equations and the circuit output are as follows. Here DA is the D input of the D-flip flop of A, and JB, KB is the J and K input of the JK-flip flop of B.


$$DA = \sim xy + yB$$

$$JB = \sim yB + xy$$


$$KB = xB + \sim yA$$

$$z = x + \sim xy$$

 1) Draw the logic diagram of the circuit and test it with Logisim.




 2) Construct a state diagram of this circuit.



Q4. (10 points) Design a system with the following state changes: This is a sequential circuit with three flip-flops. The state sequence is changed with a clock as in the order of, 111, 010, 100,110, 001, 011, 101, 000, 111 and repeat. Use JK flip-flops.

1) Draw a state diagram.

 

2) Construct an excitation table.

A_t	B_t	C_t	$A_{(t+1)}$	$B_{(t+1)}$	$C_{(t+1)}$	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	1	1	1	1	x	1	x	1	x
0	0	1	0	1	1	0	x	1	x	x	0
0	1	0	1	0	0	1	x	x	1	0	x
0	1	1	1	0	1	1	x	x	1	x	0
1	0	0	1	1	0	x	0	1	x	0	x
1	0	1	0	0	0	x	1	0	x	x	1
1	1	0	0	0	1	x	1	x	1	1	x
1	1	1	0	1	0	x	1	x	0	x	1

3) Draw K-maps and derive Boolean equations using K-maps. Make the equations as simple as possible.

J_A	AB	$\sim AB$	$\sim A \sim B$	$A \sim B$
C	x	1		x
$\sim C$	x	1	1	x

$$J_A = B + \sim C$$

K_A	AB	$\sim AB$	$\sim A \sim B$	$A \sim B$
C	1	x	x	1
$\sim C$	1	x	x	

$$K_A = B + C$$

J_B	AB	$\sim AB$	$\sim A \sim B$	$A \sim B$
C	x	x	1	
$\sim C$	x	x	1	1

$$J_B = \sim A + \sim C$$

K_B	AB	$\sim AB$	$\sim A \sim B$	$A \sim B$
C		1	x	x
$\sim C$	1	1	x	x

$$K_B = \sim A + \sim C$$


J_C	AB	$\sim AB$	$\sim A \sim B$	$A \sim B$
C	x	x	x	x
$\sim C$	1		1	

$$J_C = AB + \sim A \sim B$$

K_C	AB	$\sim AB$	$\sim A \sim B$	$A \sim B$
C	1			1
$\sim C$	x	x	x	x

$$K_C = A$$

 4) Draw the system in Logisim simulator, attach the circuit image and submit the circuit file.



5) Test the system and **attach the generated table**.

Logisim: Log main of HW#5Q4

File Edit Project Simulate Window Help

Selection Table File

A	B	C	Clock(390,480)
1	1	1	1
1	1	1	0
0	1	0	1
0	1	0	0
1	0	0	1
1	0	0	0
1	1	0	1
1	1	0	0
0	0	1	1
0	0	1	0
0	1	1	1
0	1	1	0
1	0	1	1
1	0	1	0
0	0	0	1
0	0	0	0
1	1	1	1

Close Window

Q5. (2 points) The following circuit is a simple implementation for 4X3 memory chip. In this configuration, your memory chip has four addressable space and each data in the address is 3-bit long. In order to write/read a data into/from a specified address, you have to give a right signal to the address lines, S1 and S0.

1) **(1 point)** Suppose you want to write a data 1 0 1 to the word 3 (address 3). How you will set the values in each case?

RESET	S1	S0	Bit2	Bit1	Bit0	~WE
0	1	1	1	0	1	1

2) **(1 point)** Suppose you want to read a data from the address 1. Give the correct values in each case. If some bits do not affect, then mark as X (don't care).

RESET	S1	S0	Bit2	Bit1	Bit0	~WE
0	0	1	X	X	X	0